

(請注意!! 答題務必按題號順序)

1. Answer the following questions as briefly as possible.

- (a) For the Zener diode circuit in Fig.1(a), does the R_S have the maximum or minimum value? how about the R_L ? (6%)
- (b) For a PN junction (diode) under reverse bias, will the diffusion current I_{diff} increase or decrease or not change? How about the drift current I_{drift} ? (6%)
- (c) For a n-channel MOSFET with body effect, if the bias voltage of source to substrate is increased, then the threshold voltage V_t of it will increase or decrease or not change? (3%)

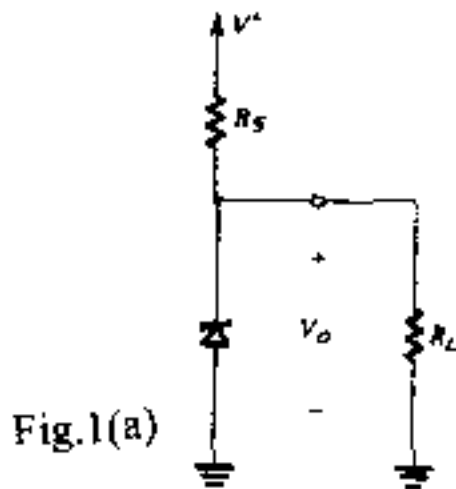


Fig.1(a)

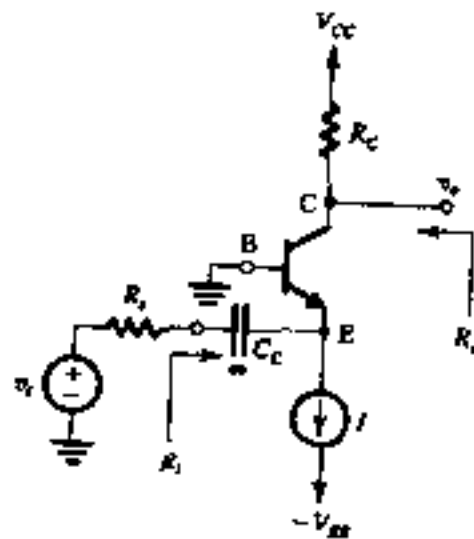


Fig.2

- 2. For the BJT in Fig.2 with $\beta = 100$, $g_m = 40 \text{ mA/V}$, $r_o = \infty$, find the voltage gain V_o/V_s , input resistance R_i , and output resistance R_o . (9%)
- 3. Sketch a cascode current mirror circuit using MOSFET, and find the output resistance R_o of it. (10%)
- 4. For Fig.4, the MOSFET with $C_{gs} = C_{gd} = 1 \text{ pF}$, $g_m = 4 \text{ mA/V}$, $r_o = \infty$. Approximately, find the mid-frequency voltage gain A_M , low 3-db frequency f_L , high 3-db frequency f_H . (16%)



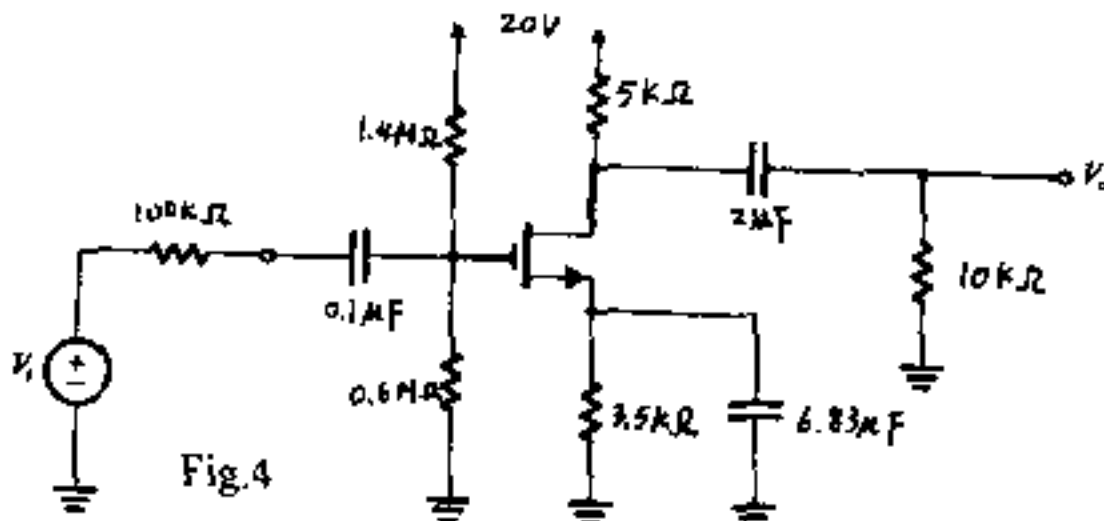


Fig.4

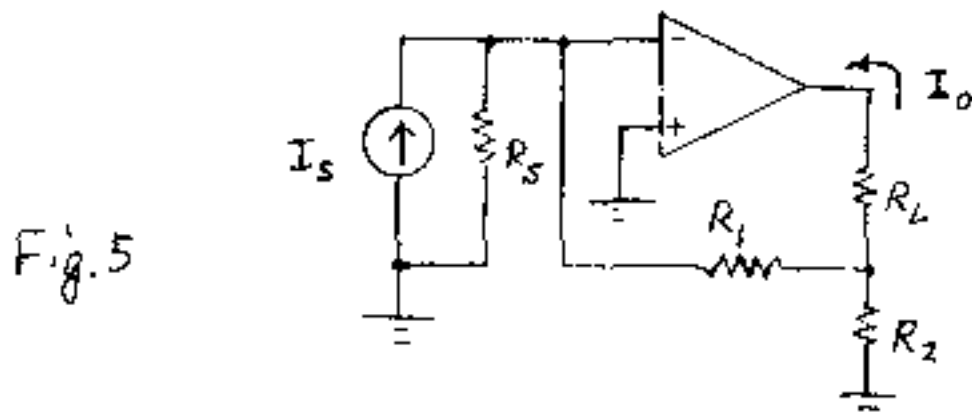
5. Show that for the circuit in Fig. 5, the current gain I_o/I_s is independent of R_L . (10%)



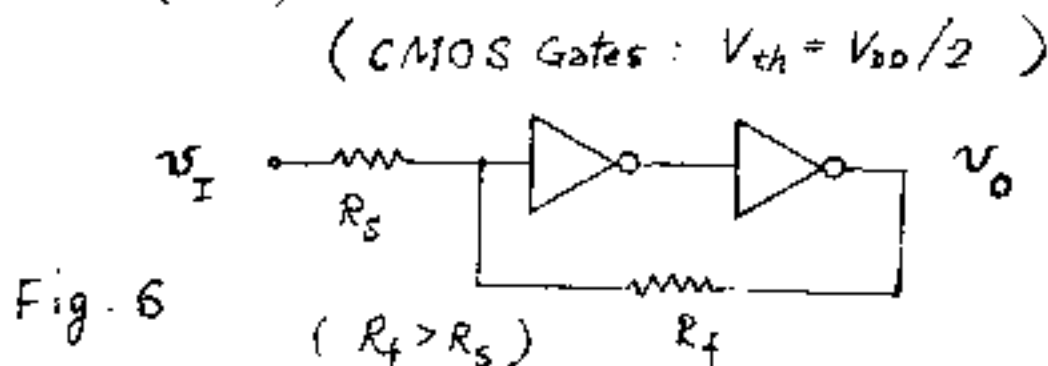6. Find the voltage transfer characteristic for the circuit shown in Fig. 6. (10%)



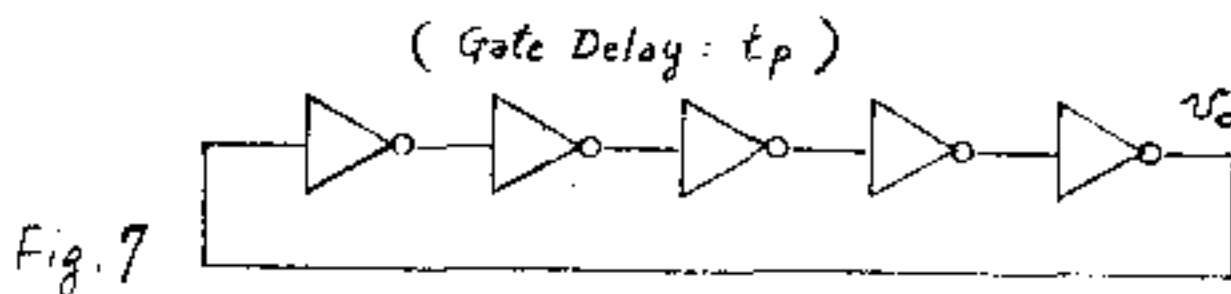7. What is the waveform of the output? (10%)



8. Sketch the waveforms at the points shown in Fig. 8. (20%)

- (a) $R_s \gg R$
 (b) $R_s = 0$

