

國 立 清 華 大 學 命 題 紙

95 學年度 電機領域聯合招生 系 ( 所 ) \_\_\_\_\_ 組碩士班入學考試

科目 電子學 科目代碼 9904 共 3 頁第 1 頁 \*請在試卷【答案卷】內作答

1. (25%) Please mark 1A(a), 1A(b), ..., 1A(e), 1B(a), and 1B(b), respectively, in top of your answers.

(1A) In a typical driver circuit as shown in Fig. 1, the zener diodes  $D_z$  are ideal with zener voltage  $V_z = 5.3\text{ V}$  and forward cut-in voltage  $V_f = 0.7\text{ V}$ . The operational amplifier is ideal too. The BJTs,  $Q_N$  and  $Q_P$ , can be modeled by  $|V_{BE(on)}| = 0.7\text{ V}$ . The power supply is  $V_{CC} = 15\text{ V}$ . The resistors are  $R = 1\text{ k}\Omega$  and  $R_L = 10\ \Omega$ . The switch SW can be selected either in position 1 or position 2. A current signal  $I_i$  with average  $I_{av}$  and peak-to-peak  $I_{pp}$  is applied to the input.

(a) When SW is at position 2, find the small signal gain  $V_L/I_i$ . (3%)

(Case 1) When  $I_i$  is a saw-tooth waveform with  $I_{av} = 0$  and  $I_{pp} = 10\text{ mA}$ ,

(b) plot the waveform of  $V_L$  for SW being at position 1. (3%)

(c) plot the waveform of  $V_L$  for SW being at position 2. (3%)

(Case 2) When  $I_i$  is a saw-tooth waveform with  $I_{av} = 0$  and  $I_{pp} = 20\text{ mA}$ ,

(d) plot the waveform of  $V_L$  for SW being at position 1. (3%)

(e) plot the waveform of  $V_L$  for SW being at position 2. (3%)

Note: Be sure to properly indicate the voltage values in your plots.

 


Fig. 1

(1B) A Si-BJT with  $\beta = 100$  and  $r_o = \infty$  is used to make a common emitter amplifier biased by a constant current source as shown in Fig. 2. The capacitance  $C$  is very large.

(a) Sketch the small signal equivalent circuit for this amplifier using hybrid- $\pi$ -model. (4%)

(b) If a voltage gain of  $V_o/V_i = -200$  is desired, find the value of  $I_Q$  and the input resistance  $R_{in}$ . (6%)

 


Fig. 2

95 學年度 電機領域聯合招生 系 (所) \_\_\_\_\_ 組碩士班入學考試

科目 電子學 科目代碼 9904 共 3 頁第 2 頁 \*請在試卷【答案卷】內作答

2. (25%) A 2-stage amplifier with an equivalent circuit is shown in Fig. 3. Let  $A_{v1}=100$ ,  $A_{v2}=100$ ,  $C_1=C_2=0.1\text{pF}$  and the resistance at node X, Y are  $R_X=R_Y=1\text{M}\Omega$ .

- (a) If  $C_M=0$ , write down the transfer function of the overall gain,  $A_v(\omega)$ . (5%)
- (b) Sketch both the gain and phase Bode plots of this amplifier. (5%)
- (c) With Miller compensation,  $C_M=10\text{pF}$ , find the new dominant pole,  $\omega_{pD}$ . (5%)
- (d) Sketch the Bode plots (gain and phase) of the amplifier with  $C_M=10\text{pF}$ . Estimate the unity gain bandwidth and the phase margin,  $\phi_M$  and label them in your plots. (10%)


 


Fig. 3

3. (25%)

 (a) For a CMOS linear amplifier as shown below, what are the operation modes of  $Q_N$  and  $Q_P$  in BC and CD regions, respectively? (Ans: off or triode or saturation)? (8%)



(b) As shown above with  $v_I=0$  V, please sketch the  $i_{DN}$  and  $i_{DP}$  vs  $v_O$  curves. Please indicate the operation point and  $V_{OH}$ . (9%)

(c) In memory circuit, should the Word and Bit lines be connected to source/drain, gate, or substrate of MOSFET, respectively? (4%)

(d) What are the approximate dimensions (in cm) of channel length and gate oxide thickness of MOSFET in current VLSI, respectively? (4%)

4. (25%) Consisted of a Schottky diode, two resistors, and three BJTs, a modified ECL with three inputs  $A$ ,  $B$ ,  $V_R$  and an output  $C$  is described as follows. Two primary inputs  $A$ ,  $B$  and a reference voltage  $V_R$  are connected to the bases of BJT  $Q_2$ ,  $Q_1$ , and  $Q_3$ , respectively; All the emitters of BJT  $Q_1$ ,  $Q_2$ , and  $Q_3$  are connected to node  $E$ , and the first resistor  $R_E$  are wired between node  $E$  and ground; Both the collectors of BJT  $Q_1$  and  $Q_2$  are wired to power supply  $V_{CC}$ , while the collector of BJT  $Q_3$  is the output  $C$ . The Schottky diode and the second resistor  $R_C$  are wired in parallel between power supply  $V_{CC}$  and output  $C$ .

(a) Please draw this modified ECL circuit. (10%)

(b) Write the output function  $C$  in terms of inputs  $A$  and  $B$  with brief explanation. (6%)

(c) Find voltages of  $V_R$ , logic-0 and logic-1 in terms of  $V_{CC}$  and  $V_\gamma$ , where  $V_\gamma$  is the turn-on voltage of the Schottky diode. (9%)