 


1. A MOS differential amplifier utilized a bias current $I=25\mu\text{A}$. The devices have $V_t=1\text{V}$, $W=120\mu\text{m}$, $L=6\mu\text{m}$ and $\mu_n C_{ox}$ for this technology is $20\mu\text{A}/\text{V}^2$. Find V_{GS} , g_m , and the differential input voltage v_{id} for full current switching. (15%)

2. A non-inverting amplifier is constructed with $R_2=100\Omega$ and R_f adjustable. The op amp open-loop gain is $A_{OL}=10\alpha^3/[(s+\alpha)(s+2\alpha)^2]$

(a) Find the value of R_f that will just place one of the closed-loop amplifier poles at $s=-3\alpha$. (5%)

(b) For the value of R_f chosen in part (a), what are the locations of the other two amplifier poles? (10%)




3. (25%) A BJT with $\beta=100$ is used in the circuit below with the voltage $V_{BE}=0.7\text{V}$.

(a) Determine the voltage V_{CB} and the transconductance g_m of the BJT. (8%)

(b) Sketch the small signal equivalent circuit. (7%)

 (c) Find the voltage gain V_o/V_s and the input resistance R_i . (10%)



4. (10%) As shown in the Fig. 3, calculate V_o by neglect R_{sc} (Assuming that op amp 741 is ideal).

5. (20%) As shown in the Fig. 3, a voltage regulator is used to provide constant voltage V_o with maximum output current $I_o = 0.5$ A. The V_{BE} turn-on voltage for Q2 and Q3 are, respectively, 0.6V and 0.7V (at 25°C), respectively, with the $\partial V_{BE3(on)} / \partial T = -2.5$ mV/°C

- (a) Calculate the minimum load. (5%)
- (b) At what temperature (°C) this voltage regulator will be thermal shut down? (5%)
- (c) Mark the protection elements (5%)
- (d) Calculate R_{sc} by neglect voltage over R2. (5%)

 


Fig. 3

6. (a) Draw the structure of a CMOS transmission gate in transistor level with each transistor as 4-node device (5%)

(b) Explain the operations if the values of the control signal are VDD and Ground. (10%)