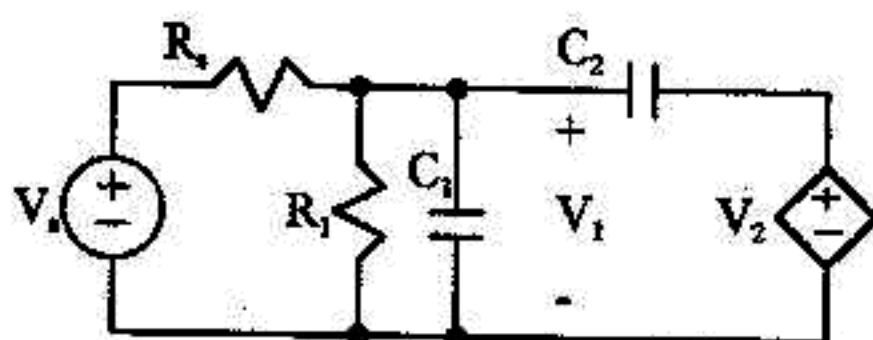


1. A signal source V_s with output resistance R_s is connected in the circuit as shown.

It is known that the voltage V_2 is induced by the voltage V_1 such that $V_2 = kV_1$.


- (1) Derive an expression for the transfer function V_1/V_s .
- (2) Find the expression for pole frequency f_H .
- (3) If $R_1 = R_s = 1\text{k}\Omega$, $C_1 = 20\text{pF}$, $C_2 = 2\text{pF}$, and $k = -9$, sketch the Bode plot for $|V_1/V_s|$. (15%)



2.(1) Sketch the circuit of a cascode amplifier using two identical BJTs.

- (2) What are the input resistance, output resistance, and voltage gain of your circuit?
- (3) What is the advantage of this amplifier as compared to a common emitter amplifier? (10%)

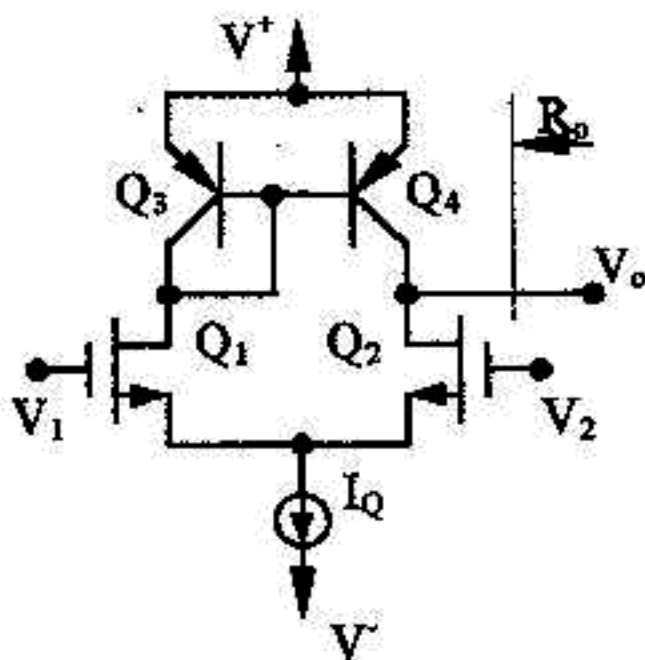
3. In the BiCMOS differential amplifier as shown, $I_Q = 0.6\text{mA}$, $k_n = 0.3\text{mA/V}^2$, $\lambda = 0.01\text{V}^{-1}$ for the MOSFETs; $V_A = 80\text{V}$ for the BJTs. Find the output resistance R_o , the differential input resistance, and the voltage gain $A_d = v_o/(v_2 - v_1)$. (10%)



八十八學年度 電子工程 系(所) 組碩士班研究生招生考試


科目 電子學 科號 4702 共 3 頁第 2 頁 *請在試卷【答案卷】內作答

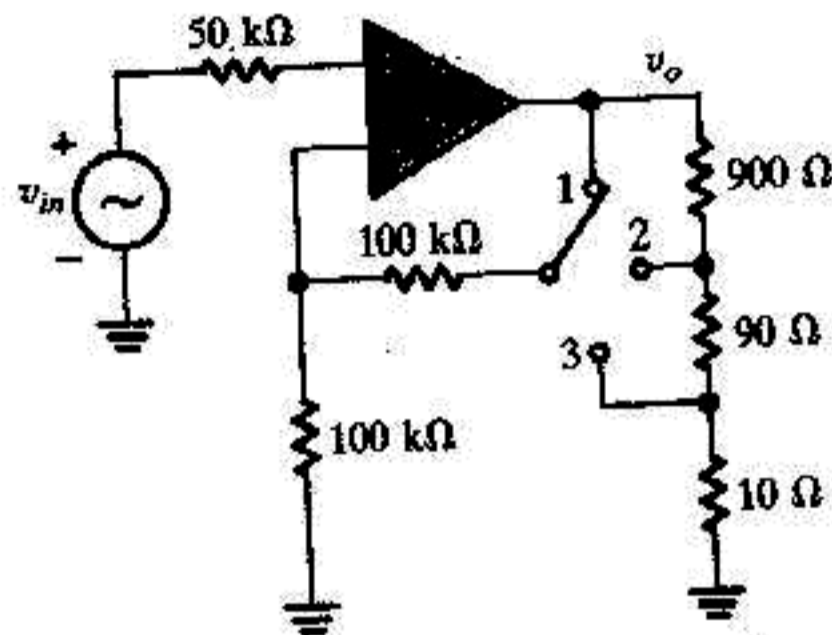4. Find the voltage gain of the following circuit with the switch in positions 1, 2, and 3. (15%)



5. An amplifier with inverting circuit intended for very-high-frequency operation, yet characterized by a single-pole roll-off, has $f_t = 100\text{MHz}$ and $A_{v0} = 20\text{V/V}$. For a design in which the actual (rather than the nominal) closed-loop gain is -10V/V , what 3dB frequency results? (10%)

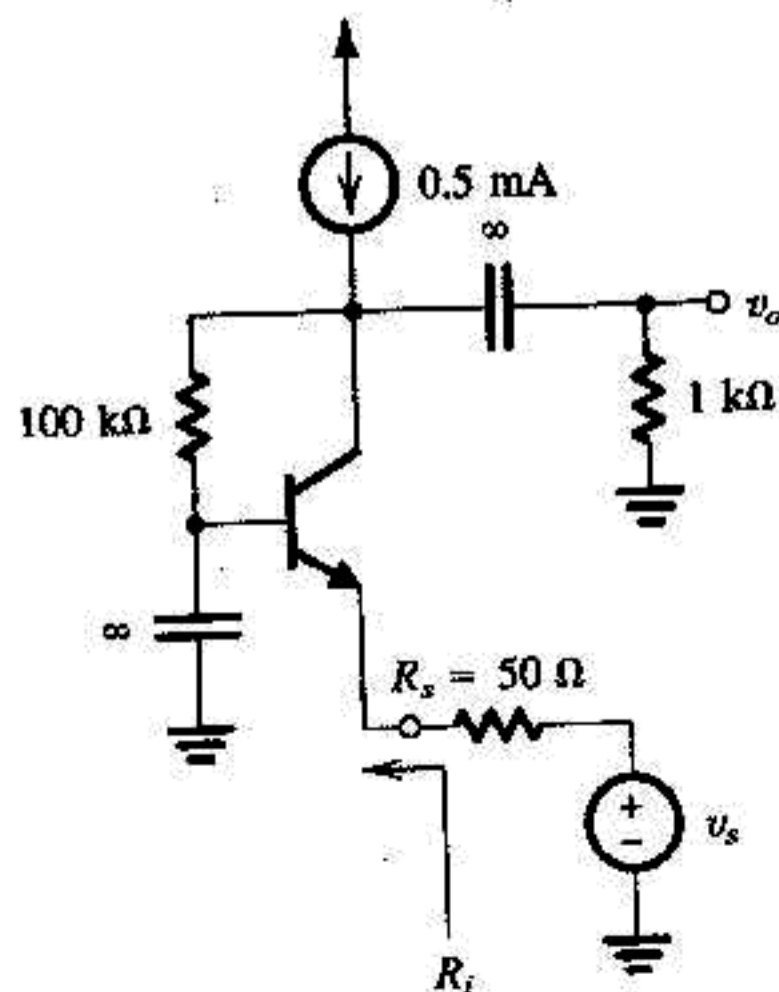
6. For the circuit shown, find the input resistance R_i , and the voltage gain v_o/v_s . Assume that the source provides a small signal v_s , and that β is high. Note that a transistor remains in the active region even if the collector voltage falls below that of the base by 0.4V or so. (10%)



八十八學年度 電子工程 系(所) 組碩士班研究生招生考試

科目 電子學 科號 4702 共 3 頁第 3 頁 *請在試卷【答案卷】內作答

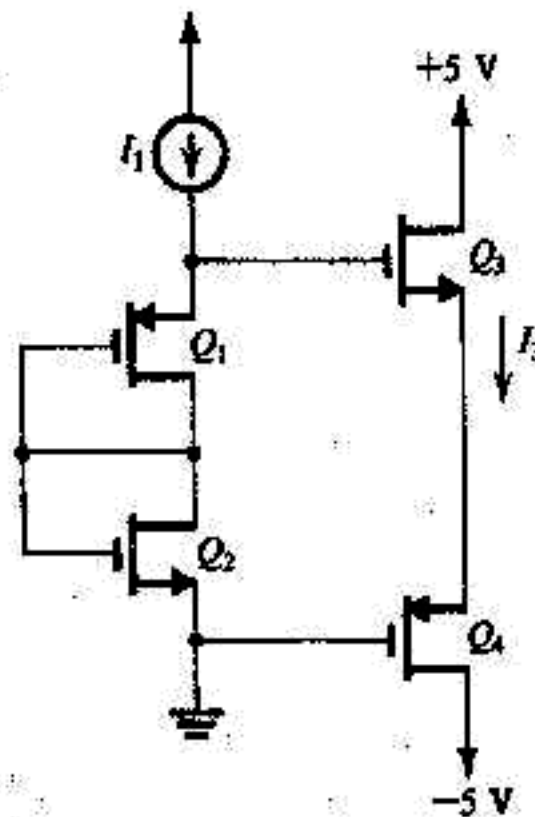7. Assuming the threshold voltage of all devices to be equal in magnitude and k denotes $(1/2)(\mu C_{ox} W/L)$. If $k_1=k_2$, and $k_3=k_4=16k_1$, find the required value of I_1 such that $I_3=1.6\text{mA}$. (15%)



8. Find the transfer function $V_o(s)/V_i(s)$ of the following circuit. Sketch the Bode plot for both gain and phase angle. (15%)

