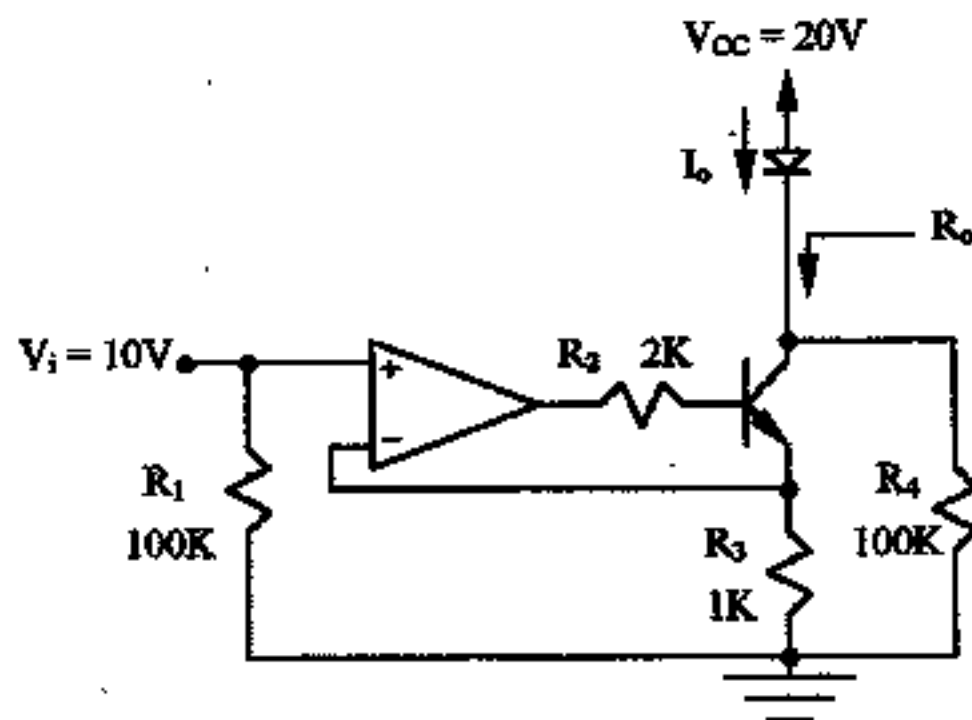



1. The op-amp in the circuit is ideal and the BJT has $\beta = 99$. The forward voltage drop of the diode is $V_D = 0.7\text{ V}$.

- (1) Calculate the current I_o . (6%)
- (2) Find the output resistance R_o . (6%)




2. The MOSFET parameters in the circuit are $k_n = 1\text{ mA/V}^2$, $V_{TH} = 1\text{ V}$.


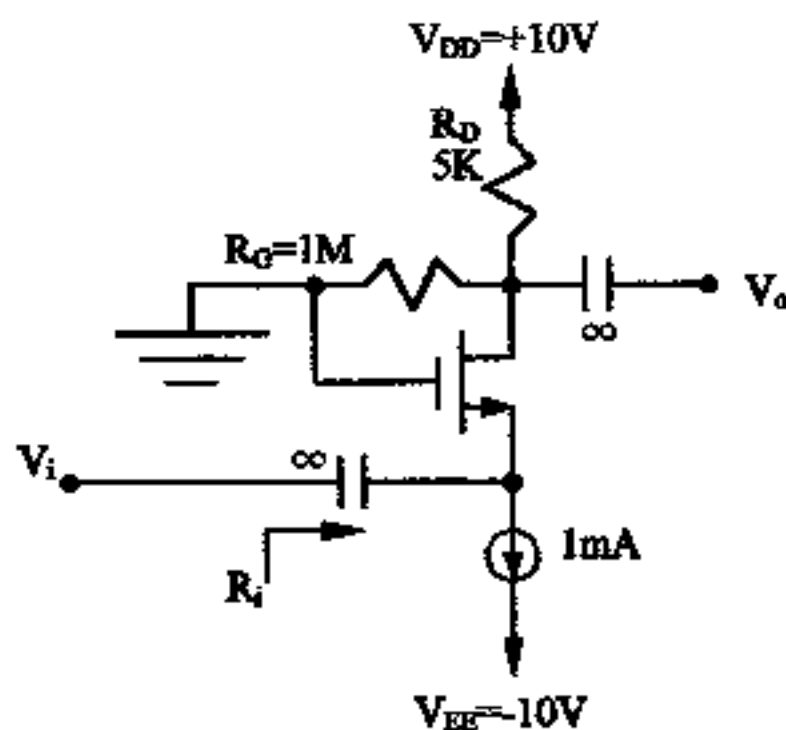
- (1) Calculate the values V_{DS} and g_m of the MOSFET. (8%)
- (2) Sketch the small signal equivalent circuit. (3%)
- (3) Find the voltage gain V_o/V_i and input resistance R_i . (7%)



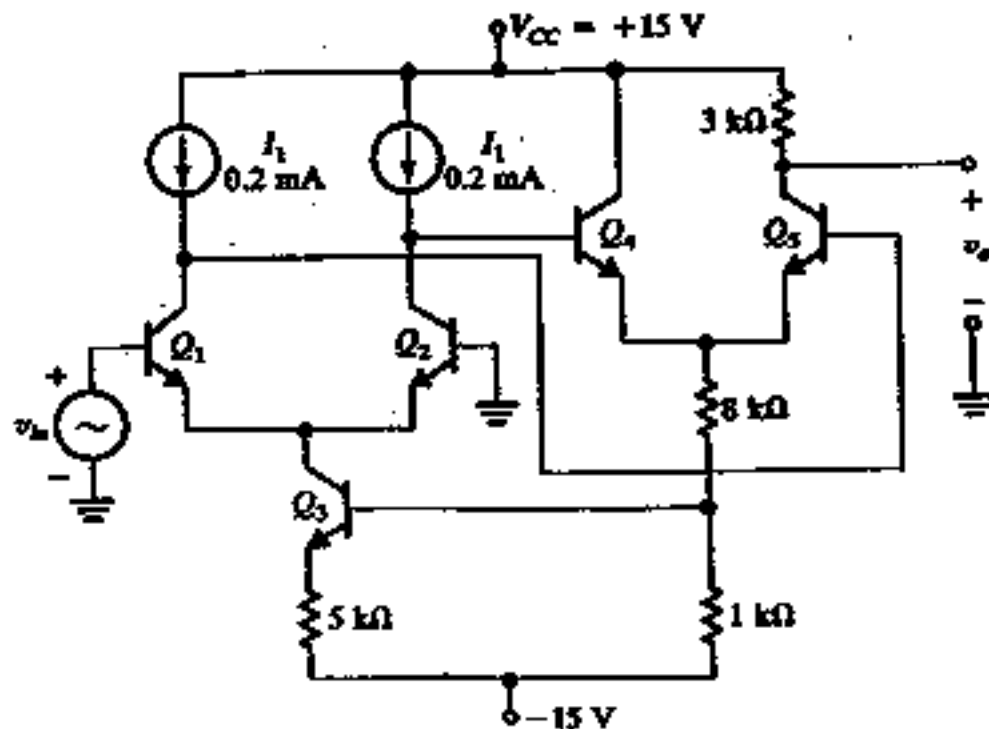3. For the following circuit, $r_{\pi} = 1\text{k}\Omega$, and $\beta = 100$ for all BJTs. (a) Determine the dc values of V_O and V_{CE5} if $v_{in} = 0$, $I_{B4} \neq 0$, and $I_{B5} \neq 0$. (8%) (b) Find the small-signal ac gain v_o/v_{in} . (7%)



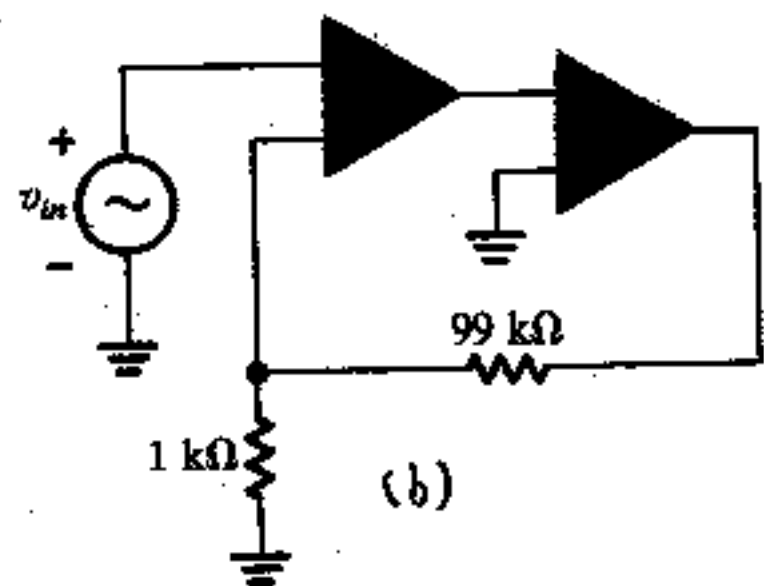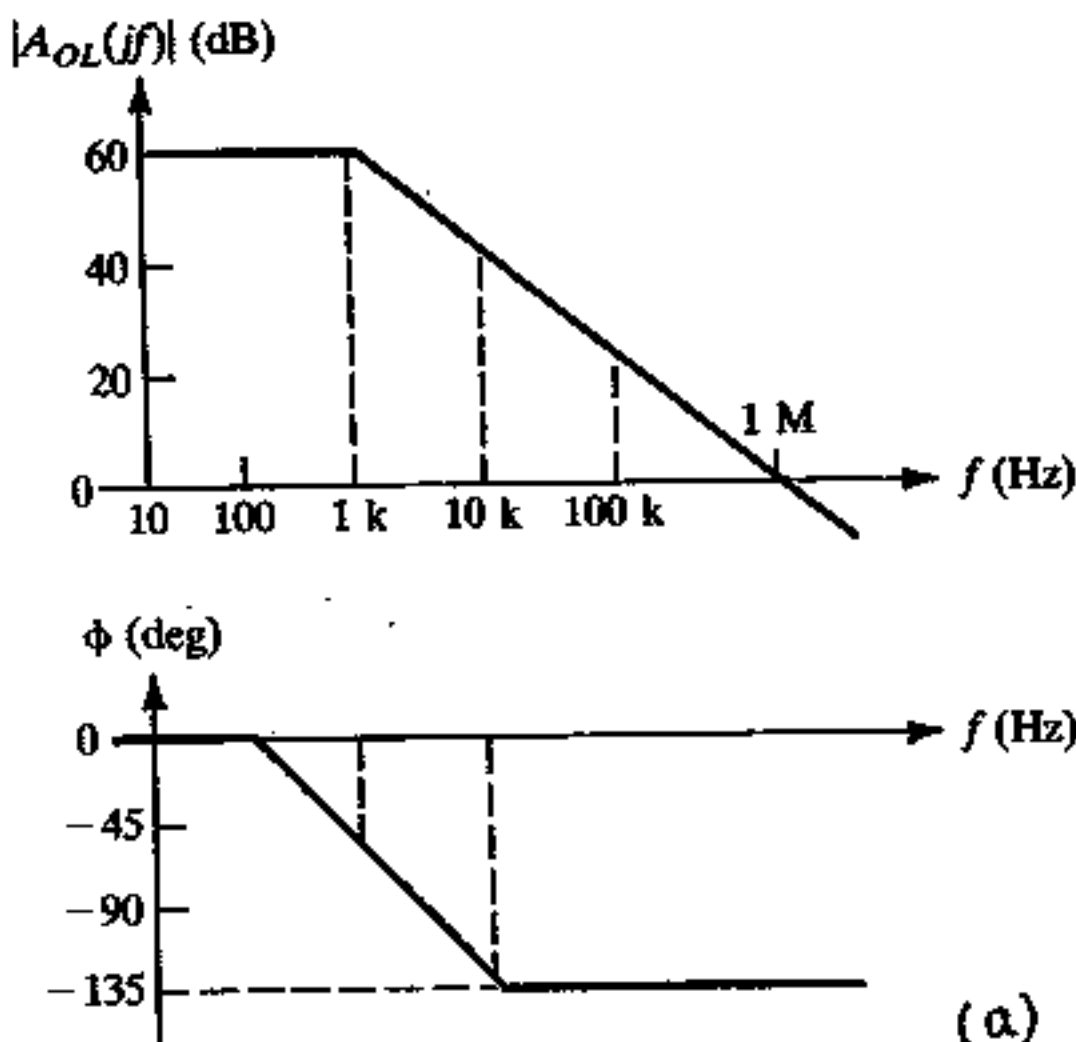
4. If the A_{OL} gain-phase characteristics are shown in Fig.(a), determine the overall stability of the circuit shown in Fig. (b). (15%)



(a)

(b)

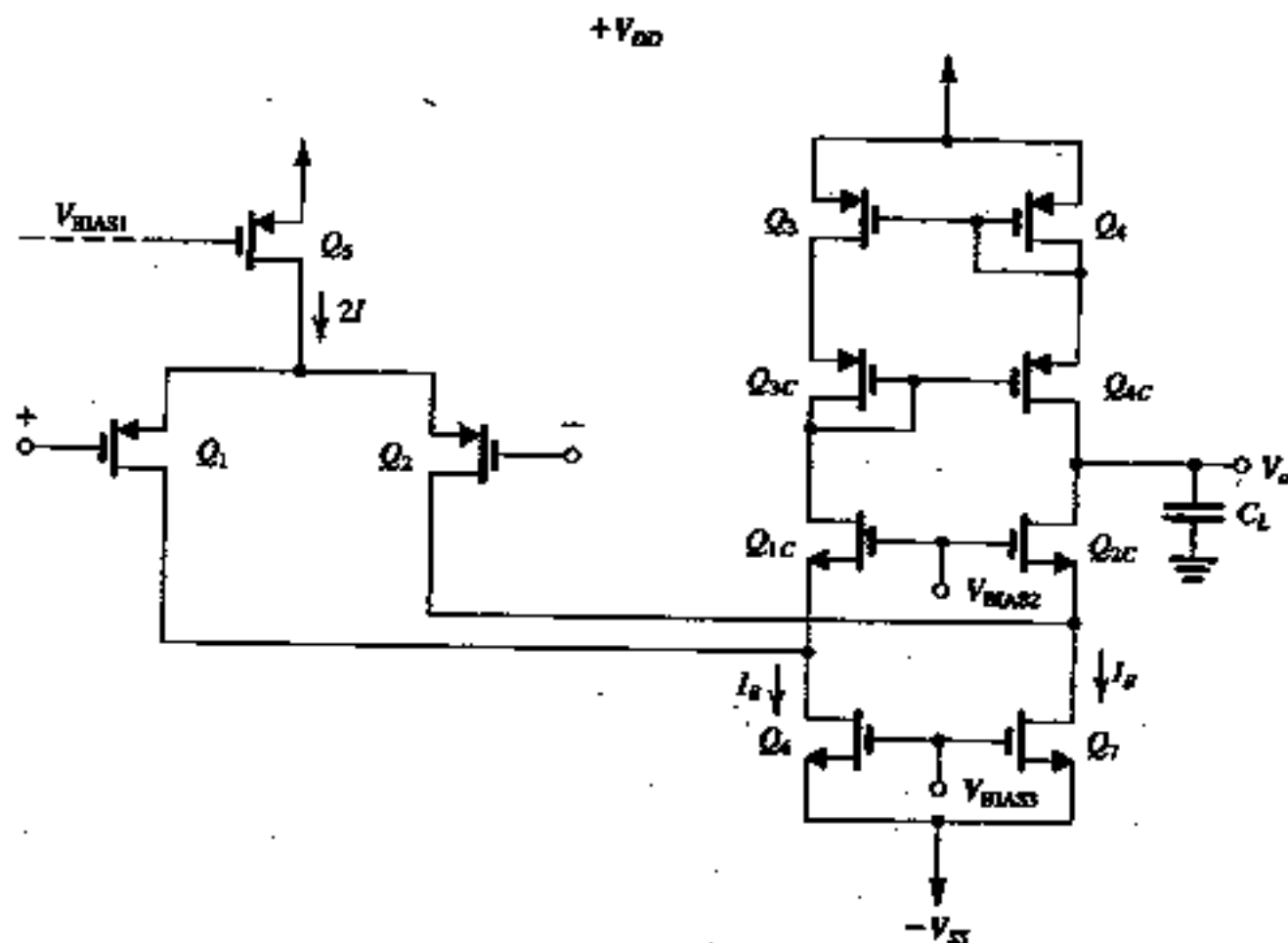5. Describe the important features of the circuit shown below, and explain how does this circuit obtain the superior performance over conventional-structured amplifiers. (20%)



6. For the following circuit the diodes have a constant 0.7V drop when conducting, and the op-amp saturates at $\pm 10V$. (a) Sketch and label the transfer characteristic v_o-v_i and find the maximum diode current. (10%) (b) Redo part (a) with R_1 eliminated and R_2 short-circuited. (10%)

